

A circuit comprises a 2 henry inductor, a $20\ \Omega$ resistor, and a $1/338$ farad capacitor. The initial charge stored on the capacitor is -4 Coulombs and the initial current is $+56$ amps. Obtain the solution for charge $q(t)$.

Given:

$$\begin{aligned} L &= 2\ \text{h}, & C &= 1/338\ \text{f}, & R &= 20\ \Omega, \\ q(0) &= -4, & q'(0) &= i(0) = +56. \end{aligned}$$

There is no voltage source, so the ODE (governing equation) is then

$$Lq'' + Rq' + \frac{1}{C}q = 0 \quad \implies \quad 2q'' + 20q' + 338q = 0. \quad (1)$$

The characteristic equation

$$m^2 + 10m + 169 = 0$$

has roots

$$m_{1,2} = -5 \pm 12i,$$

so the general solution is

$$q(t) = e^{-5t}(c_1 \cos 12t + c_2 \sin 12t). \quad (2)$$

Then

$$q'(t) = -5e^{-5t}(c_1 \cos 12t + c_2 \sin 12t) + e^{-5t}(-12c_1 \sin 12t + 12c_2 \cos 12t). \quad (3)$$

Initial Conditions:

From equations (2) and (3) we obtain

$$\begin{aligned} q(0) &= e^0(c_1 \cos 0 + c_2 \sin 0), \\ -4 &= c_1, \end{aligned} \quad (4)$$

$$\begin{aligned} q'(0) &= -5e^0(c_1 \cos 0 + c_2 \sin 0) + e^0(-12c_1 \sin 0 + 12c_2 \cos 0), \\ +56 &= -5c_1 + 12c_2. \end{aligned} \quad (5)$$

We solve equations (4) and (5) for c_1 and c_2 to obtain $c_1 = -4$ and $c_2 = 3$. So the solution is

$$q(t) = e^{-5t}(-4 \cos 12t + 3 \sin 12t). \quad (6)$$

NOTE: The period is

$$T = \frac{2\pi}{12} = \frac{\pi}{6} \text{ sec/cycle}.$$

NOTES:

1. Recall that the current is

$$i(t) \equiv q'(t) = \dots$$

2. This is exactly Example 4 handed out in Section 5.1.2.