

A circuit comprises a 1 henry inductor and a 0.25 farad capacitor. There is no resistor. Initially  $q(0) = 0$  and  $i(0) = 0$ , but there is an impressed voltage of  $E(t) = 24 \sin 4t$ . Obtain the charge  $q(t)$ .

Given:

$$\begin{aligned} L &= 1 \text{ h}, & R &= 0 \Omega, & C &= 0.25 \text{ f}, \\ q(0) &= 0, & q'(0) &= i(0) = 0. \end{aligned}$$

The nonhomogeneous ODE (governing equation) is then

$$L q'' + R q' + \frac{1}{C} q = E(t) \quad \implies \quad q'' + 4 q = 24 \sin 4t. \quad (1)$$

### STEP 1: COMPLEMENTARY SOLUTION

The characteristic equation

$$m^2 + 4 = 0$$

has roots

$$m_{1,2} = \pm 2i.$$

So the complementary solution is (see Sec. 5.1.1)

$$q_c(t) = c_1 \cos 2t + c_2 \sin 2t. \quad (2)$$

### STEP 2: PARTICULAR SOLUTION

Now we seek a particular solution of (1). We'll use **undetermined coefficients**:

Input Function:	Terms
$E = 24 \sin 4t$	$\sin 4t$
$E' = 96 \cos 4t$	$\cos 4t$
$E'' = -284 \sin 4t$	$\sin 4t$
List: $\cos 4t, \sin 4t$	

$\mathcal{Q}$ : Do any terms in the List already appear in  $x_c$ ?

$\mathcal{A}$ : No, so we need not modify the List.

So we seek a particular solution of (1) that is a linear combination of terms in the List:

$$q_p = a \cos 4t + b \sin 4t. \quad (3)$$

We substitute  $q_p$  into (1) and collect like terms to obtain

$$-12a \cos 4t + -12b \sin 4t \equiv 24 \sin 4t.$$

Equate like terms:

$$\begin{aligned} \cos 4t : \quad -12a &\equiv 0 \quad \implies \quad a = 0 \\ \sin 4t : \quad -12b &\equiv 24 \quad \implies \quad b = -2 \end{aligned}$$

So by (3), a particular solution of (1) is

$$q_p(t) = -2 \sin 4t. \quad (4)$$

---

### STEP 3: GENERAL SOLUTION

Then the general solution of the nonhomogeneous problem (1) is

$$\begin{aligned} q(t) &= q_c + q_p \\ &= c_1 \cos 2t + c_2 \sin 2t - 2 \sin 4t. \end{aligned} \quad (5)$$

and

$$q'(t) = -2c_1 \sin 2t + 2c_2 \cos 2t - 8 \cos 4t \quad (6)$$

---

### STEP 4: APPLY INITIAL CONDITIONS:

From equations (5) and (6) we obtain

$$q(0) = c_1 \equiv 0, \quad (7)$$

$$q'(0) = 2c_2 - 8 \equiv 0 \implies c_2 = 4. \quad (8)$$

So by (5), the solution is

$$\text{charge: } q(t) = 4 \sin 2t - 2 \sin 4t, \quad (9)$$

$$\text{current: } i(t) \equiv q'(t) = 8 \cos 2t - 8 \cos 4t.$$

---

### NOTES & NEW CONCEPTS:

1. In this example, the complementary solution  $q_c(t) = c_1 \cos 2t + c_2 \sin 2t$  represents *simple harmonic motion*, (i.e., constant amplitude oscillation) with *natural frequency*

$$f = \frac{2}{2\pi} = \frac{1}{\pi} \text{ Hz}.$$

2. In this example, the particular solution  $q_p(t) = -2 \sin 4t$  also represents *simple harmonic motion*, (i.e., constant amplitude oscillation) with frequency

$$f = \frac{4}{2\pi} = \frac{2}{\pi} \text{ Hz}.$$

Note also that the frequency of the particular solution IS the frequency of the voltage  $E(t)$ .

3. This problem is exactly Example 6 that was handed out in Section 5.1.3.